

2 to 4 Line Decoder

Structural 程序代写代做 CS编程辅导




WeChat: cstutorcs

Assignment Project Exam Help

Email: tutores@163.com

QQ: 749389476

<https://tutorcs.com>

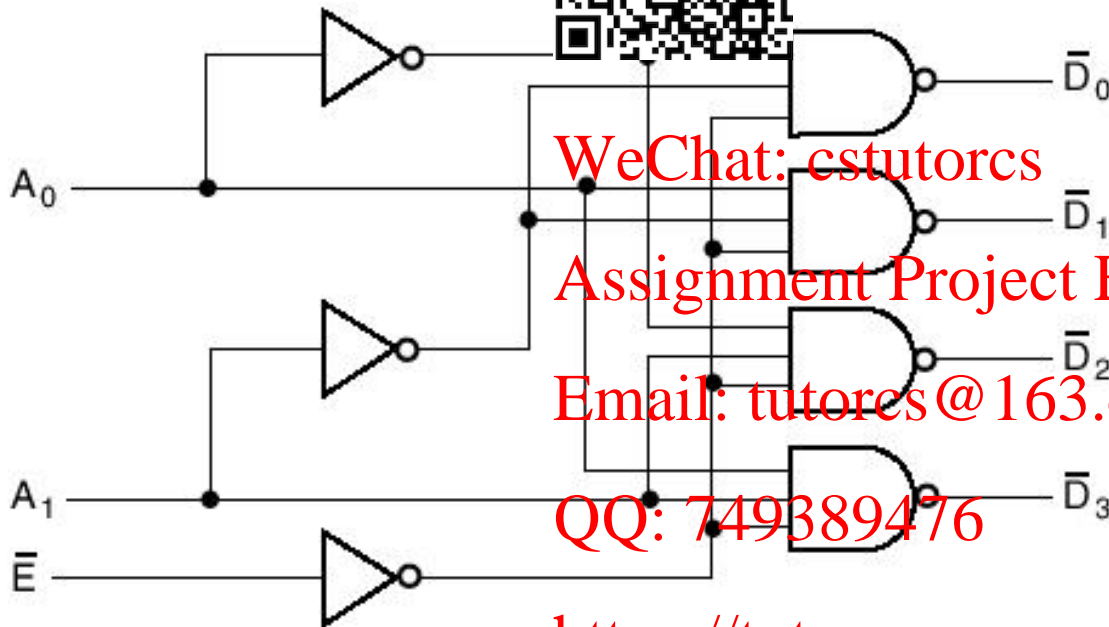

\bar{E}	A_1	A_0	\bar{D}_0	\bar{D}_1	\bar{D}_2	\bar{D}_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1

(b) Truth table

$$\bar{D}_0 = \overline{E \bar{A}_1 \bar{A}_0}$$

$$\bar{D}_1 = \overline{E \bar{A}_1 A_0}$$

$$\bar{D}_2 = \overline{E A_1 \bar{A}_0}$$

$$\bar{D}_3 = \overline{E A_1 A_0}$$

2 to 4 Line Decoder (Page 1)

Structural VHDL Description



-- 2-to-4 Line Decoder Structural VHDL Description
library ieee;

use ieee.std_logic_1164.all, lcdh_vhdl.func_prims.all;

entity decoder_2_to_4 is
port(E, A0, A1: in std_logic;
D0, D1, D2, D3: out std_logic);

end decoder_2_to_4;

architecture structural_1 of decoder_2_to_4 is

component NOT1
port(in1: in std_logic;
out1: out std_logic);

end component;

WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

https://tutorcs.com

2 to 4 Line Decoder (Page 3)

程序代写代做 CS编程辅导



```
component  
  port(in1, out1, out2, out3);  
end component;
```

```
signal not_A0, not_A1; std_logic;  
begin
```

```
g0: NOT1 port map (in1 => A0, out1 => not_A0);
```

```
g1: NOT1 port map (in1 => A1, out1 => not_A1);
```

```
g2: NAND3 port map (in1 => not_A0, in2 => not_A1,  
                    in3 => E, out1 => D0);
```

```
g3: NAND3 port map (in1 => A0, in2 => not_A1,  
                    in3 => E, out1 => D1);
```

```
g4: NAND3 port map (in1 => not_A0, in2 => A1,  
                    in3 => E, out1 => D2);
```

```
g5: NAND3 port map (in1 => A0, in2 => A1,  
                    in3 => E, out1 => D3);
```

```
end structural_1;
```

WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

4 to 1 Line Multiplexer

程序代写代做CS编程辅导



WeChat: cstutorcs

Assignment Project Exam Help


Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

Function table

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

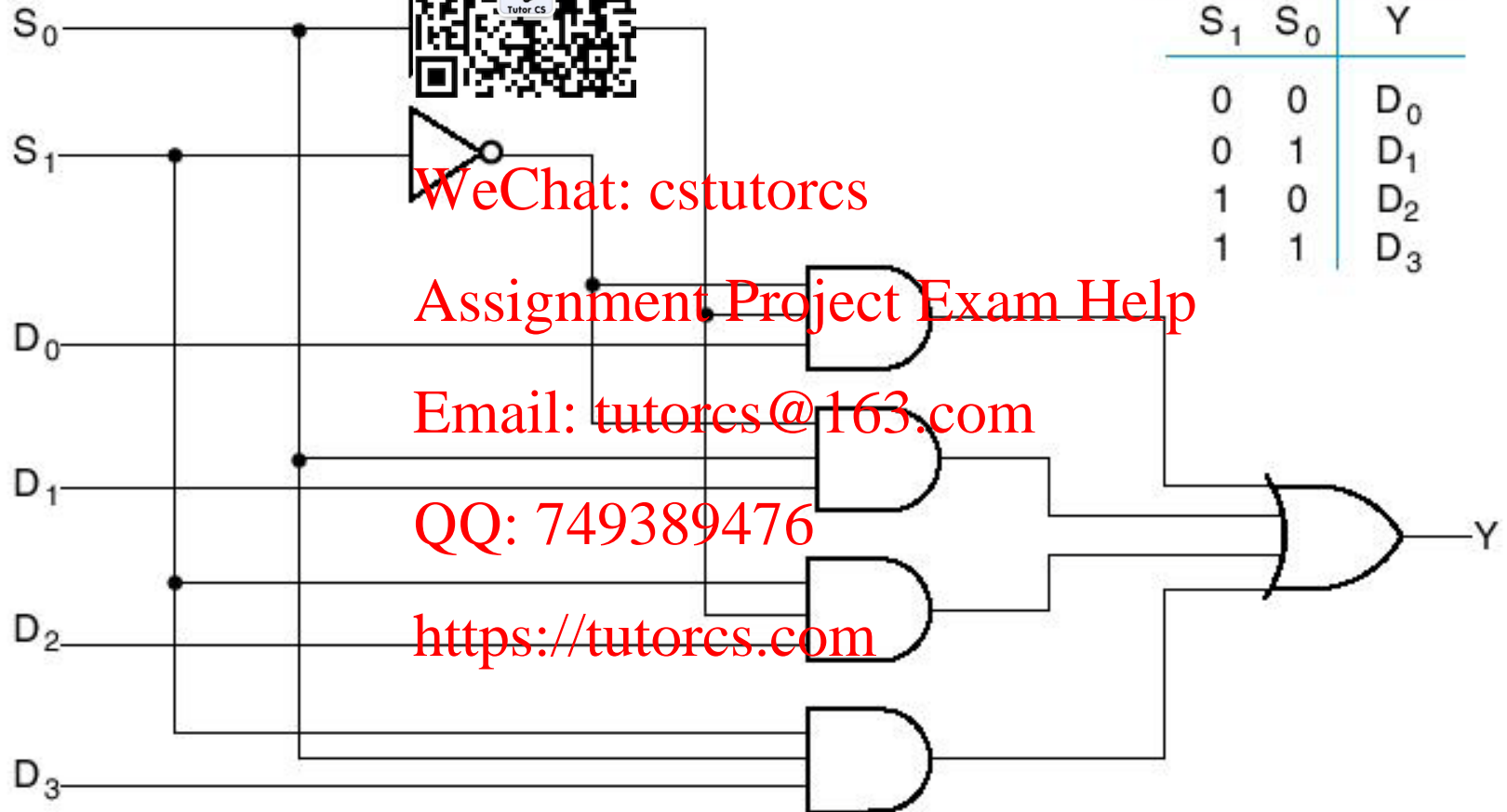

4 to 1 Line Multiplexer (Page 1)

程序代写代做 CS编程辅导



-- 4-to-1 Line Multiplexer: Structural VHDL Description

```
library ieee;  
use ieee.std_logic_1164.all, lcdf_vhdl.func_prims.all;  
entity multiplexer_4_to_1_st is
```

```
    port(S: in std_logic_vector(0 to 1);  
          D: in std_logic_vector(0 to 3);  
          Y: out std_logic);
```

```
end multiplexer_4_to_1_st;
```

```
architecture structural_2 of multiplexer_4_to_1_st is  
    component NOT1
```

```
        port(in1: in std_logic;  
              out1: out std_logic);
```

```
    end component;
```

```
    component AND3
```

```
        port(in1, in2, in3: in std_logic;  
              out1: out std_logic);
```

```
    end component;
```

WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

4 to 1 Line Multiplexer (Page 2)

程序代写代做 CS编程辅导



```
component  
  port(in1, in std_logic;  
        out1: out std_logic);  
end component;
```

WeChat: cstutorcs

```
signal not_S: std_logic_vector(0 to 1);  
signal N: std_logic_vector(0 to 3);  
begin
```

```
  g0: NOT1 port map (S(0), not_S(0));  
  g1: NOT1 port map (S(1), not_S(1));  
  g2: AND3 port map (not_S(1), not_S(0), D(0), N(0));  
  g3: AND3 port map (not_S(1), S(0), D(1), N(1));  
  g4: AND3 port map (S(1), not_S(0), D(2), N(2));  
  g5: AND3 port map (S(1), S(0), D(3), N(3));  
  g6: OR4 port map (N(0), N(1), N(2), N(3), Y);  
end structural_2;
```

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

2 to 4 Line Decoder

程序代写代做CS编程辅导

Same as slide 1




WeChat: cstutorcs

Assignment Project Exam Help

Email: tutores@163.com

QQ: 749389476

<https://tutorcs.com>

 

\bar{E}	A_1	A_0	\bar{D}_0	\bar{D}_1	\bar{D}_2	\bar{D}_3
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	x	x	1	1	1	1

(b) Truth table

$$\bar{D}_0 = \overline{E \bar{A}_1 \bar{A}_0}$$

$$\bar{D}_1 = \overline{E \bar{A}_1 A_0}$$

$$\bar{D}_2 = \overline{E A_1 \bar{A}_0}$$

$$\bar{D}_3 = \overline{E A_1 A_0}$$

2 to 4 Line Decoder(Page 1)

Dataflow 程序代写代做 CS编程辅导



-- 2-to-4 Line Decoder Dataflow VHDL Description

```
library ieee;
use ieee.std_logic_1164.all, lcdv_vhdl.func_prims.all;
entity decoder_2_to_4 is
    port(E, A0, A1: in std_logic;
         D0, D1, D2, D3: out std_logic);
end decoder_2_to_4;
```

Assignment Project Exam Help

```
architecture dataflow_1 of decoder_2_to_4 is
```

```
    signal not_A0, not_A1: std_logic;
begin
```

```
    not_A0 <= not A0;
    not_A1 <= not A1;
    D0 <= not (not_A0 and not_A1 and E);
    D1 <= not (A0 and not_A1 and E);
    D2 <= not (not_A0 and A1 and E);
    D3 <= not (A0 and A1 and E);
```

```
end dataflow_1;
```


4 to 1 Line Multiplexer

Conditional Dataflow (When-Else)

Same as slide 4



WeChat: cstutorcs

Assignment Project Exam Help


Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

Function table

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

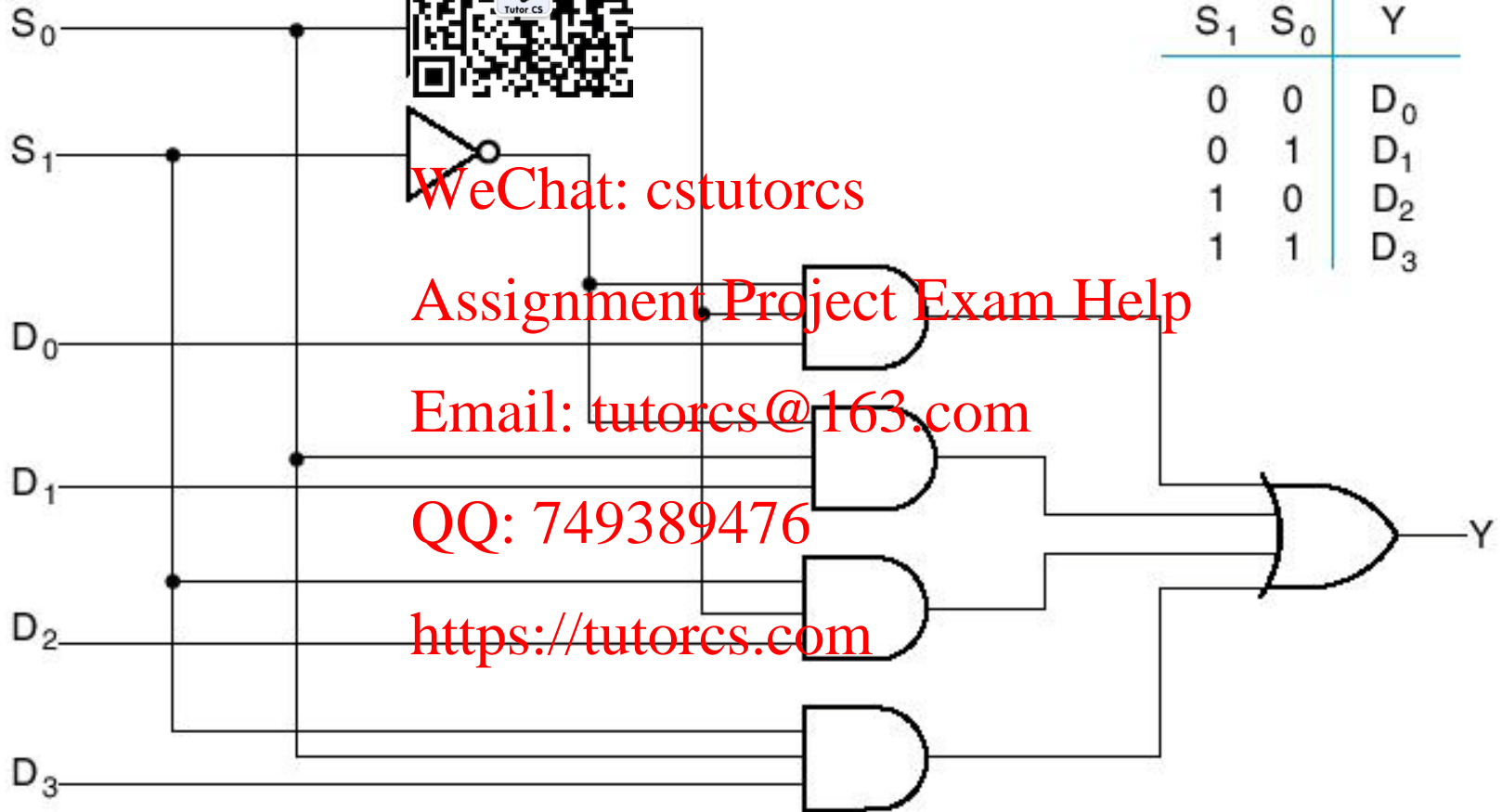

4 to 1 Line Multiplexer (Page 1)

Conditional Dataflow (When-Else)



```
library ieee;
use ieee.std_logic_1164.all;
entity multiplexer_4_to_1_we is
    port (S : in std_logic_vector(1 downto 0);
          D : in std_logic_vector(3 downto 0);
          Y : out std_logic);
end multiplexer_4_to_1_we;

architecture function_table of multiplexer_4_to_1_we is
begin
    Y <= D(0) when S = "00" else
        D(1) when S = "01" else
        D(2) when S = "10" else
        D(3) when S = "11" else
        'X';
end function_table;
```

WeChat: cstutorcs

Assignment Project Exam Help

Email: tutormcs@163.com

QQ: 749389476

https://tutormcs.com

4 to 1 Line Multiplexer (Page 1)

Conditional Dataflow (With Select)



```
library ieee;  
use ieee.std_logic_1164.all;  
entity multiplexer_4_to_1_ws is
```

```
    port (S : in std_logic_vector(1 downto 0);  
          D : in std_logic_vector(3 downto 0);  
          Y : out std_logic);
```

```
end multiplexer_4_to_1_ws;
```

```
architecture function_table_ws of multiplexer_4_to_1_ws is  
begin
```

```
    with S select
```

```
        Y <= D(0) when "00",  
             D(1) when "01",  
             D(2) when "10",  
             D(3) when "11",  
             'X' when others;
```

```
end function_table_ws;
```

WeChat: cstutores

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>