

Hierarchical VHDL

4-Bit Ripple Carry Adder





WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

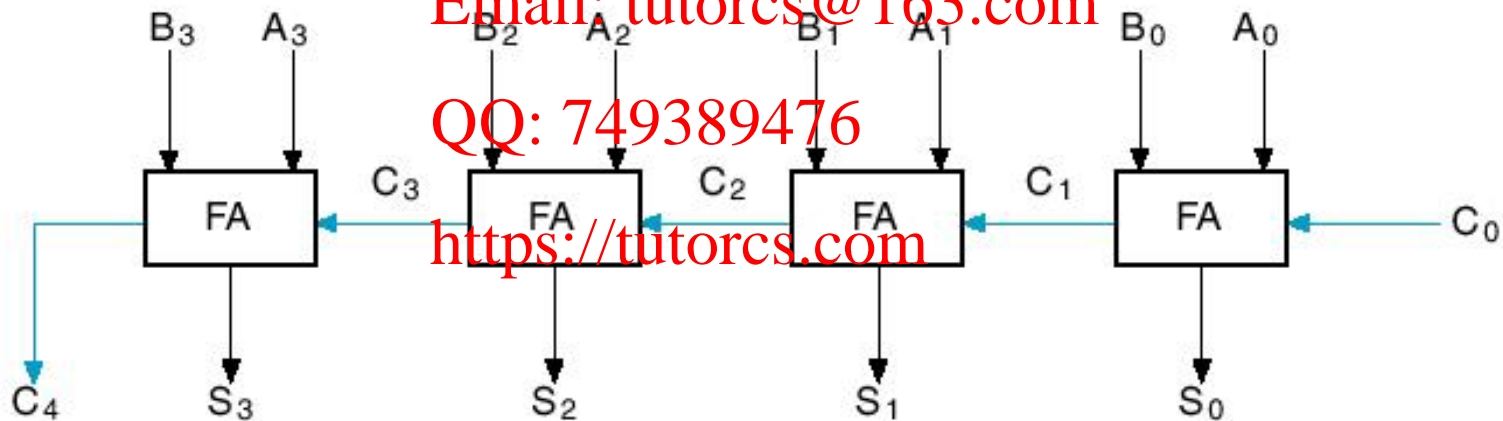 

Hierarchical VHDL (Page 1)

4-Bit 程序代码做CS编程辅导



-- 4-bit Arithmetic Dataflow/Structural library is

use ieee.std_logic_1164.all;

entity half_adder is

port (x, y : in std_logic;

s, c : out std_logic);

end half_adder;

Email: tutorcs@163.com

architecture dataflow_3 of half_adder is
begin

s <= x xor y;

c <= x and y;

end dataflow_3;

QQ: 749389476

<https://tutorcs.com>

Hierarchical VHDL (Page 2)

4-Bit 程序代码做CS编程辅导



```
library ieee;  
use ieee.std_logic_1164.all;  
entity full_adder is  
    port (x, y, z : in std_logic;  
          s, c : out std_logic);  
end full_adder;
```

WeChat: cstutorcs
Assignment Project Exam Help
Email: tutorcs@163.com
QQ: 749389476
<https://tutorcs.com>

Hierarchical VHDL (Page 3)

4-Bit 程序代码做 CS 编程辅导



```
architecture dataflow_3 of full_adder is
    component half_adder
        port(x, y : in std_logic;
             s, c : out std_logic);
    end component;
    signal hs, hc, tc : std_logic;
begin
    HA1: half_adder
        port map (x, y, hs, hc);
    HA2: half_adder
        port map (hs, z, s, tc);
    c <= tc or hc;
end struc_dataflow_3;
```

WeChat: tutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

Hierarchical VHDL (Page 4)

4-Bit 程序代码做CS编程辅导



library ieee;

use ieee.std_logic_1164.all;

entity adder_4 is

port(B, A : in std_logic_vector(3 downto 0);

C0 : in std_logic;

S : out std_logic_vector(3 downto 0);

C4 : out std_logic);

end adder_4;

<https://tutorcs.com>

Hierarchical VHDL (Page 5)

4-Bit Ripple Carry Adder



```
architecture structural_4 of adder_4 is
  component full_adder
```

```
    port(x, y, z : in std_logic;
          s, c : out std_logic);
```

```
  end component;
```

```
  signal C : std_logic_vector(3 downto 1);
```

```
begin
```

```
  Bit0: full_adder
```

```
    port map (B(0), A(0), C(0), S(0), C(1));
```

```
  Bit1: full_adder
```

```
    port map (B(1), A(1), C(1), S(1), C(2));
```

```
  Bit2: full_adder
```

```
    port map (B(2), A(2), C(2), S(2), C(3));
```

```
  Bit3: full_adder
```

```
    port map (B(3), A(3), C(3), S(3), C4);
```

```
end structural_4;
```

WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

4-Bit Full Adder

Behavioral Description



-- 4-bit Adder Behavioral Description

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;
```

```
entity adder_4_b is  
    port (B, A : in std_logic_vector(3 downto 0);  
          C0 : in std_logic;  
          S : out std_logic_vector(3 downto 0);  
          C4 : out std_logic);
```

```
end adder_4_b;
```

```
architecture behavioral of adder_4_b is  
    signal sum : std_logic_vector(4 downto 0);  
begin
```

```
    sum <= ('0' & A) + ('0' & B) + ("0000" & C0);  
    C4 <= sum(4);  
    S <= sum(3 downto 0);  
end behavioral;
```

WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

Positive Edge-Triggered D Flip-Flop

Process Description (Entity)
程序代写代做CS编程辅导



-- Positive Edge-Triggered D Flip-Flop with Reset:

-- VHDL Process Description

library ieee;

use ieee.std_logic_1164.all;

entity dff is

port(CLK, RESET, D: in std_logic;

Q, Q_n: out std_logic);

end dff;

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

Positive Edge-Triggered D Flip-Flop

Process description & CS programming



architecture of dff is

- Implements positive edge-triggered bit state storage
- with asynchronous reset.

signal state: `std_logic`;

begin WeChat: cstutorcs

Q <= state;

Q_n <= not state;

process (CLK, RESET)

begin

if (RESET = '1') then

state <= '0';

else

if ((CLK'event and CLK = '1') then

state <= D;

end if;

end if;

end process;

end;

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>