

程序代写代做 CS编程辅导 Microprogram Design



- ▶ Use ASM from Figure 16 to design the Microprograms

WeChat: cstutorcs

- ▶ See Symbolic/Binary Microprogram on next slide

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

Symbolic/Binary Microprogram



Address	NXT ADD	MS	MC					TD	TA	TB	MB	FS	MD	RW	MM	MW
IF	EX0	CNT	—	NLI	NLP	NLP	—	—	—	—	—	—	—	NW	PC	NW
EXO	—	NXT	OPC	NLI	NLP	NLP	—	—	—	—	—	—	—	NW	—	NW
ADI	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	Constant	$F = A + B$	FnUt	WR	—	NW	
LD	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	—	—	Data	WR	MA	NW	
ST	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	Register	—	—	NW	MA	WR	
INC	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	—	$F = A + 1$	FnUt	WR	—	NW	
NOT	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	—	$F = \overline{A}$	FnUt	WR	—	NW	
ADD	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	SB	Register	$F = A + B$	FnUt	WR	—	NW	

WeChat: cstutors

Assignment Project Exam Help

Address	NXT ADD	MS	MC	IL	PI	PL	TD	TA	TB	MB	FS	MD	RW	MM	MW
192	193	000	0	1	1	0	0	0	0	0	00000	0	0	1	0
193	000	001	1	0	0	0	0	0	0	0	00000	0	0	0	0
000	192	001	0	0	0	0	0	0	0	1	00010	0	1	0	0
001	192	001	0	0	0	0	0	0	0	0	00000	1	1	0	0
002	192	001	0	0	0	0	0	0	0	0	00000	0	0	0	1
003	192	001	0	0	0	0	0	0	0	0	00001	0	1	0	0
004	192	001	0	0	0	0	0	0	0	0	01110	0	1	0	0
005	192	001	0	0	0	0	0	0	0	0	00010	0	1	0	0


Email: tutors@163.com

QQ: 749389476

<https://tutorcs.com>

This is not our control memory but similar

Indirect Instruction ACM

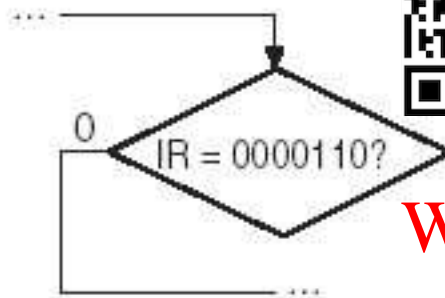


WeChat: cstutorcs

Assignment Project Exam Help


Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

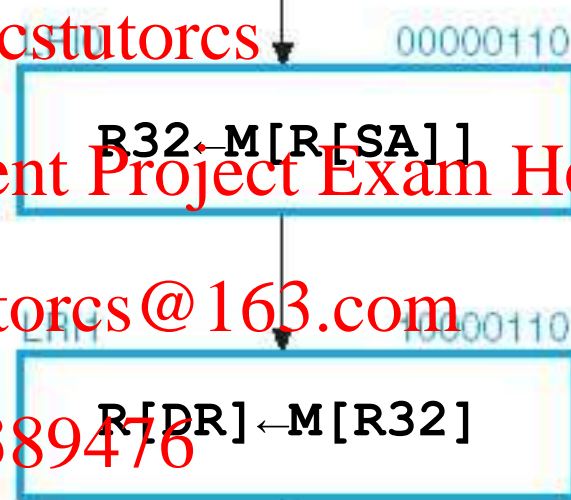


Right-Shift Instruction ASIM

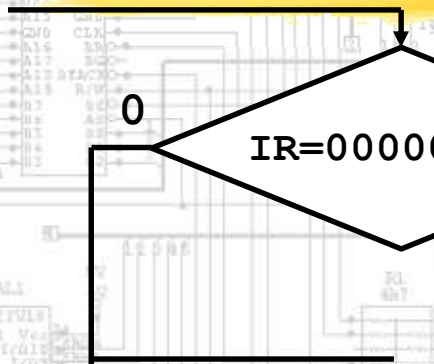

SRM1 00000111

R32 ← zf IR[4:0]

WeChat: cstutorcs

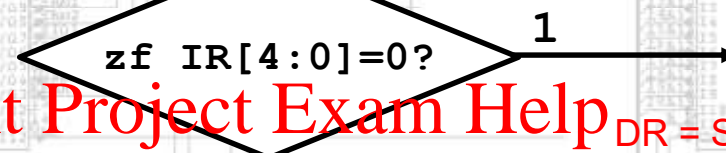

Assignment Project Exam Help

DR = SB
and
SB = Address = n sr

The number of shifts
to the right n must be
the same as the SB
register that holds the
value that will be
shifted by n bits to
the right

Email: tutorcs@163.com

QQ: 749389476


<https://tutorcs.com>

SRM2 10000111

R[DR] ← sr R[SB]

SRM3 10001000

R32 ← R32 - 1

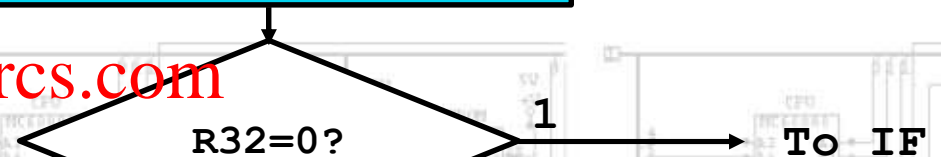

Hardwired Multiple-Cycle Control




WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

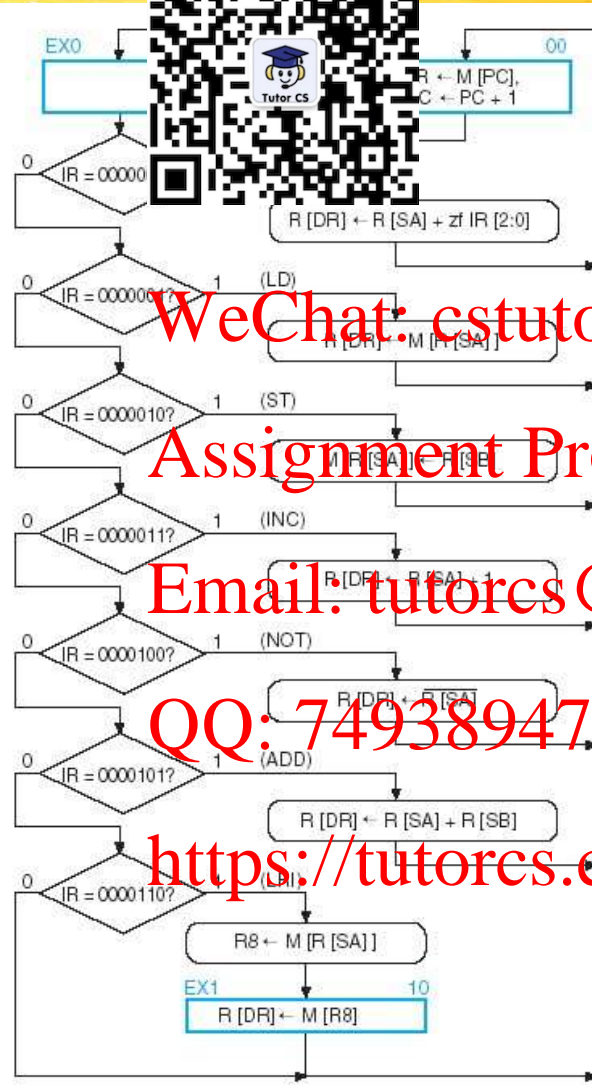

程序代写代做CS编程辅导 Hardwired Control Unit



CR

inter



WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

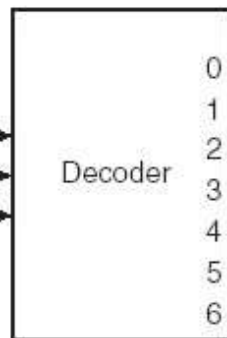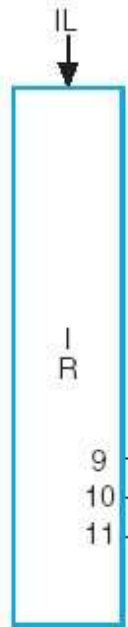

Pipelined (程序代写代做 CS编程辅导)




WeChat: cstutorcs

Assignment Project Exam Help


Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

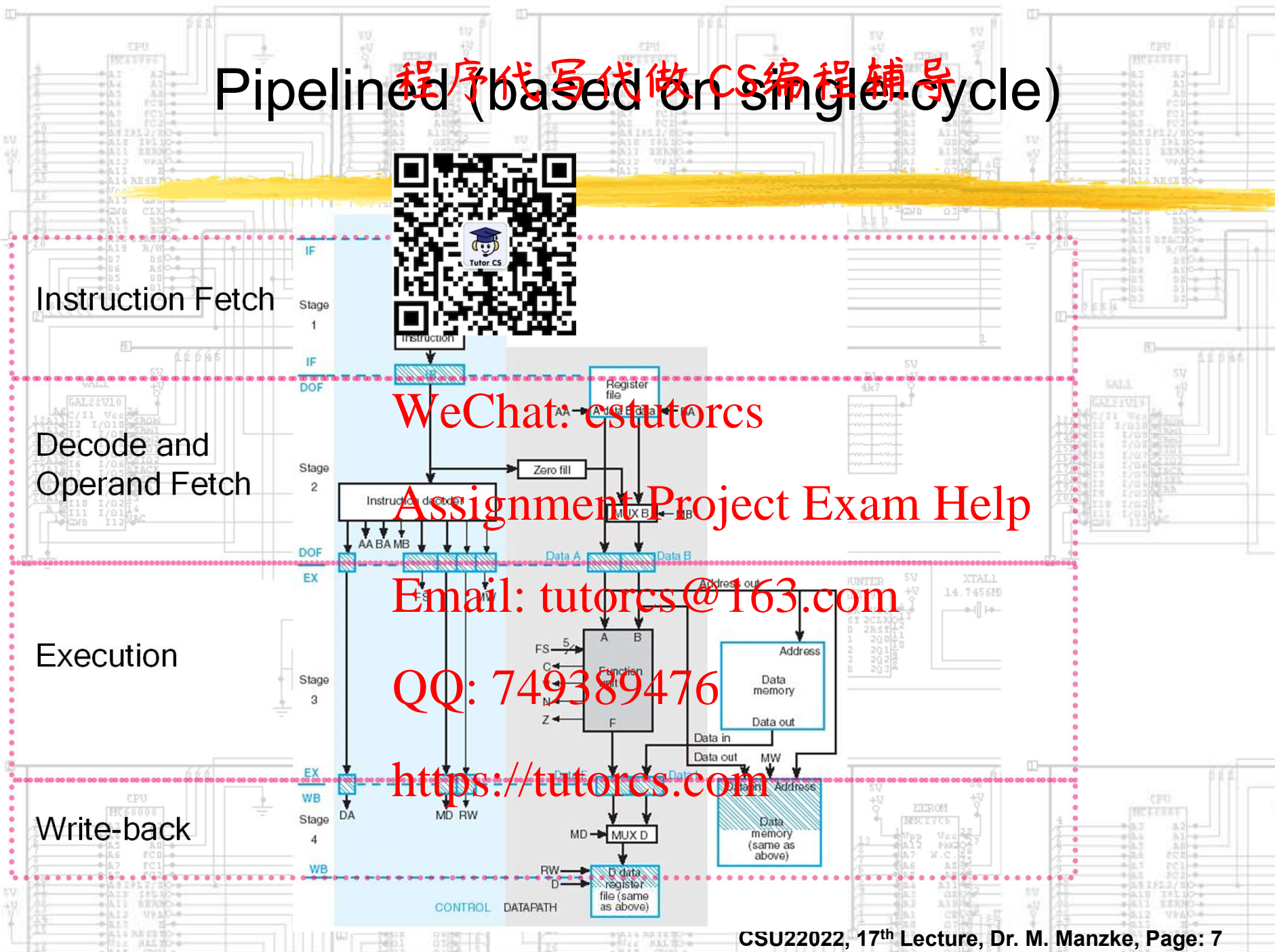

Pipeline Execution Pattern

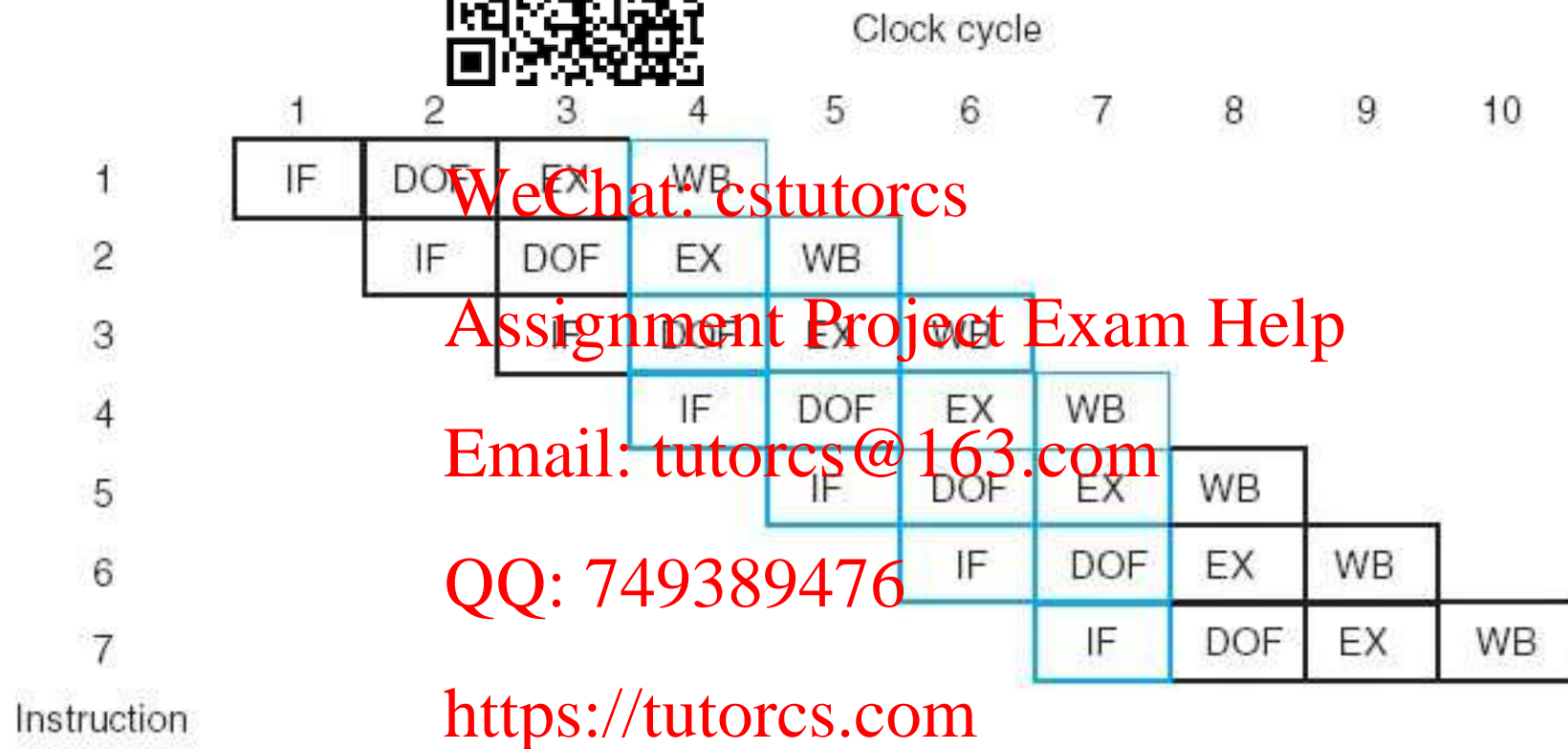

WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

Computer Architecture and Microprocessor Systems

程序代写代做 CS编程辅导



WeChat: cstutorcs

Assignment Project Exam Help

Email: tutorcs@163.com

QQ: 749389476

<https://tutorcs.com>

